

4_popquiz Power, Wattage

⚠ This is a preview of the published version of the quiz

Started: Mar 22 at 7:04pm

Quiz Instructions

Only one attempt. No makeup. Discuss with your classmates

Remember the power of a load of resistance R is $P = V^2 / R$ or $P = RI^2$ (or you can also use $P = VI$)

$P = VI$ is always true. The other equations are only true for load of resistance R



Question 1 20 pts

A toaster has a resistance of 75 ohms and is plugged into a 115V outlet.

How much current does it draw ?

Hint : see the equations in the header of the popquiz



2 A



652 mA



1.5 A



8625 mA



Question 2 20 pts

A toaster has a resistance of 75 ohms and is plugged into a 115V outlet. Use previous result.

How much does it cost if it operates for a total of 10 hours? About?

The cost of electricity is \$0.11 per KWh.

hint: \$1 = 100 cents so \$0.11 is 11 cents ! Be careful. its tricky

☐

\$2

☐

20 cents

☐

\$20

☐

\$1



Question 3 15 pts

A 40W light bulb is plugged in an outlet 120V. Its resistance is?

Hint the equations in the header of the popquiz . Find an equation with V, P and R

☐

360ohms

☐

4800ohms

☐

100 ohms

☐

3 ohms



Question 4 20 pts

a 100 W light bulb is plugged into a 120 V outlet. What is its resistance R

☐

12000 ohms

☐

14,400

☐

1.2 ohms

☐

144ohms



Question 5 1 pts

Which one has a larger resistance

40W light bulb or 100W light bulb .

See previous questions.

- ☐ Can't be determined
- ☐ They have the same resistance
- ☐ 100W
- ☐ 40W
- ☒


Question 6 15 pts

Go here.

<https://phet.colorado.edu/en/simulations/circuit-construction-kit-dc> 

(<https://phet.colorado.edu/en/simulations/circuit-construction-kit-dc>)

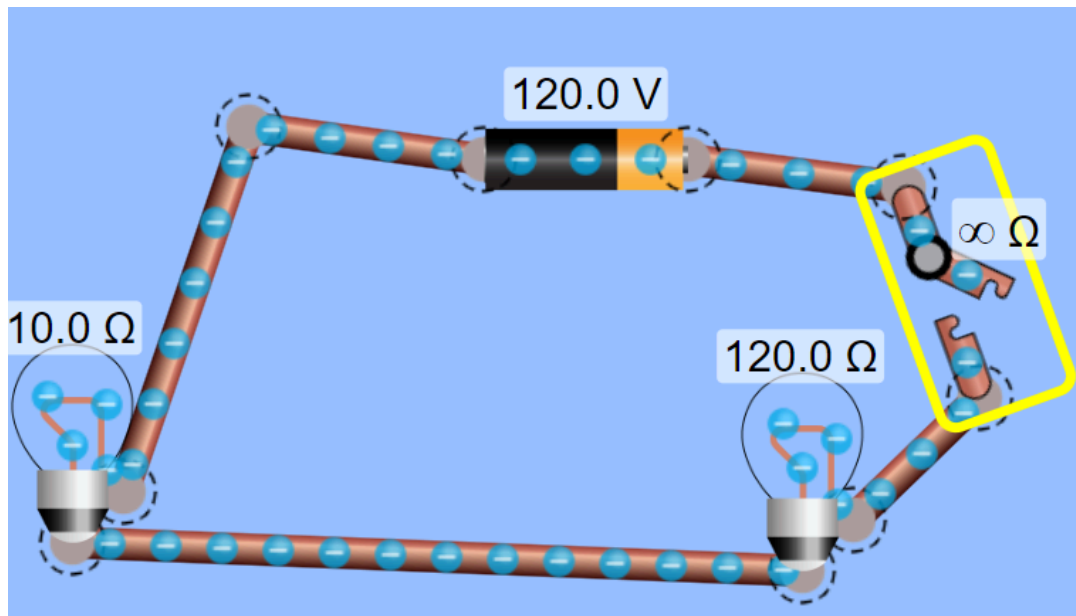Have 2 light bulbs in series with a 120V power supply. give one light bulb a very large resistance of 120 ohms and give the other one a small resistance of 10 ohms



Close the switch. Which one is the brightest ? Isn't that suprising?

- ☐ the 10 ohms is the brightest
- ☐ The 120 ohms is the brightest
- ☐ They are equally bright


☐

IDK

⋮

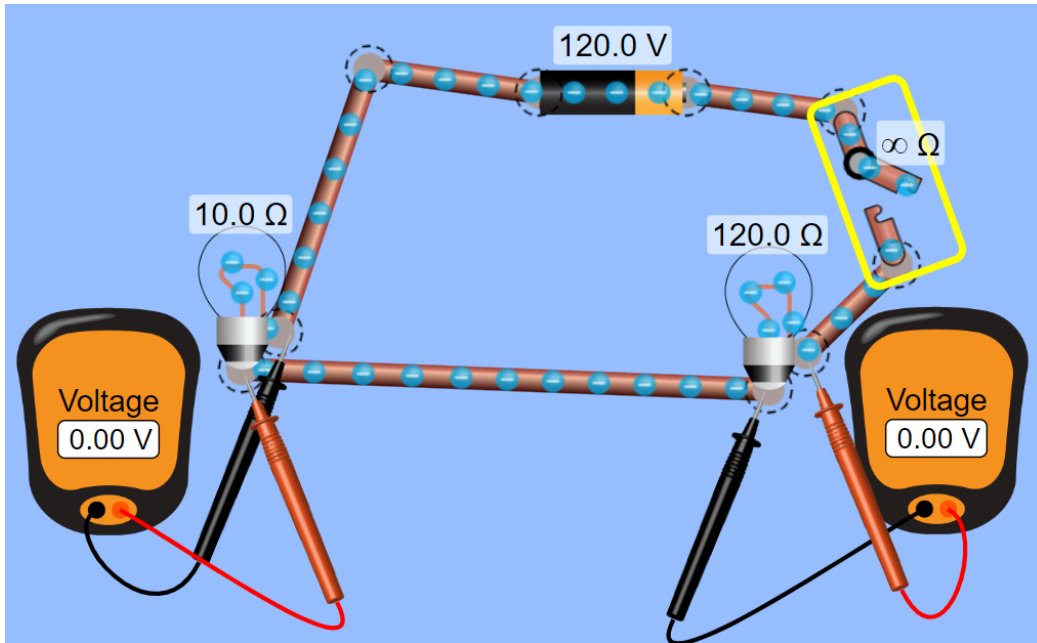Question 7 5 pts

Use the same circuit and measure the voltage across the loads:



close the switch. What is true

☐

the voltage across the 10 ohms is way larger

☐

Both load get 120V across

☐

they have about the same voltage drop

☐

The voltage across the 120 ohms is way larger

⋮

Question 8 5 pts

based on your investigations above. If you have a 40W light bulb and a 100W light bulb in series. (so 120V in series with those 2 light bulbs) then

☐

the 40W bulb will be the brightest

☐

My brain is foggy

☐

They have the same brightness

☐

The 100W will be the brightest

Not saved

Submit Quiz